Pi Hat block diagram Battery pack, Outlet used for 3 Samsung 18650's Low voltage Typical yield approximately 12 Volts LED lamp. MOSFET to control Power. **Currently using** Sparkfun 12959 Raspberry Pi zero wireless CPT 12V to USB Using A to D converters Power converter And C1205003 GPIOs. Analog to Digital Converter Multi-channel (at least 2) I2C connection. Currently using PCF8591T. GP10 to control battery power PIR Presence detector To output. **GPIO**

Pi functions used.

Pi function	Label on connector	Description
GPIO	GPIO 4	Output → Turns output to low voltage lamp off and on.
GPIO	GPIO 17	Input → PIR presence detector
A to D Converter	SDA1, SCL1 (I2C devices) PCF8591T	Ain 0 is the "ambient light level" Voltage to sensor is supplied from Pi's 3.3 V, so scaling is not required.
A to D Converter	SDA1, SCL 1 (I2C devices) PCF8591T	Ain 1 is battery voltage level scaled to 0-3.3V DC with voltage divider.